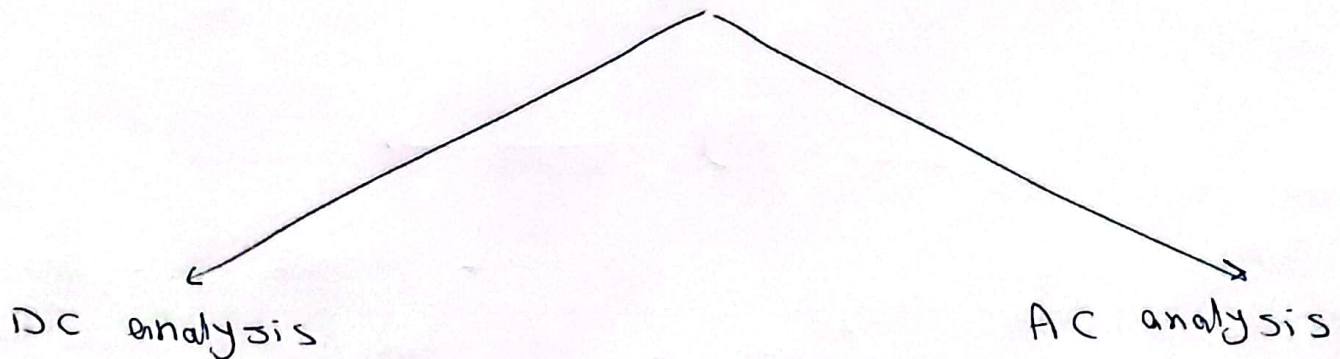


Section 1

دوائر الكترونيك

For electronic circuits' analysis, we make :-



* ac Voltage source
is replaced with
short circuit (s.c)

* ac current source
→ open circuit (o.c)

* any capacitor $X_c = \frac{1}{j\omega C}$
→ (o.c)

because $\omega = 0$

← How →

* DC Voltage source
→ (s.c)

* DC current source
→ (o.c)

* any capacitor
→ (s.c)

where $X_c = \frac{1}{j\omega C}$

≈ 0

Frequency response
يتم منبجھ التردد جيئ ائجل المكثفات في
حالة الـ ac analysis
س.ع ← جيئ ائصل على الـ
الطبيعي response
للدائرة

DC analysis

AC analysis

* Compute DC

why

Voltages :-

($V_B, V_C, V_E, V_{BE}, V_{BC}, V_{CE}$)

and DC currents :-

(I_C, I_B, I_E) then compute

$$r_e = \frac{26 \text{ mV}}{I_E}$$


$$r_o = \frac{V_A}{I_E}$$

DC Parameters of AC model

* Determine Q Point of transistor to know

in any applications (amplifier, switch \rightarrow on/off) the transistor will act as.

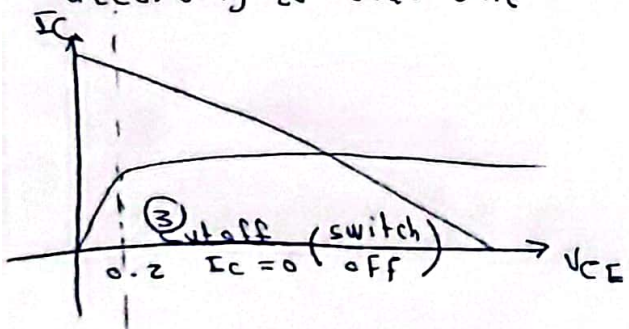* Q Point is determined according to Load Line



② Saturation
 $V_{BE}(F)$
 $V_{BC}(F)$
application
switch on

① active region

V_{BE} (Forward) and V_{BC} (Reverse)

$V_{CE} > 0.2$ and $I_C \neq 0$

application :- amplifier

CE
CC
CB

* Voltage gain (A_v)

and current gain (A_i)


For three types of amplifiers

CE
CC
CB

* input & output impedances

Z_{in} & Z_{out}

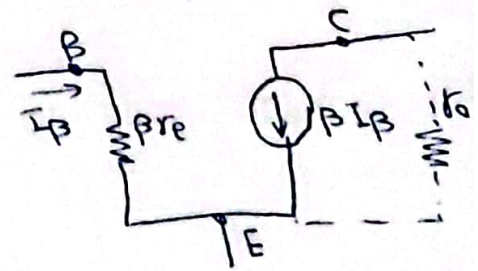where they are useful concerned the cascade circuit with multi stages in order to avoid power loss during its transferring from one stage to another.




DC Analysis of sheet 1

[1]

$$V_i(ac) \rightarrow s.c$$

$$C \rightarrow o.c$$

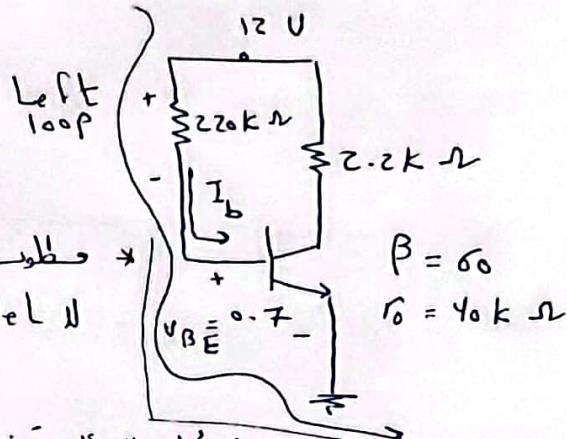* مطلوب إيجاد r_e والى بتعمل للمقاومة الداخلية
لا AC model والى مستخدمه فيما بعد لإيجاد
Gain, Z_{in} , Z_{out}



* في أول المسألة نفترض وجودها في active region لموضع

$$V_{BE} = 0.7V$$

وفي آخرها نتأكد من الفرض ده

apply kvl at left loop:-

$$12 - 220k I_b - 0.7 = 0$$

$$I_b = \frac{12 - 0.7}{220k} = 0.05mA = 51.4 \mu A$$

$$I_E = I_b + I_c = I_b + \beta I_b = (\beta + 1) I_b$$

$$I_E = (60 + 1) \times 0.05 = 3.05mA$$

$$r_e = \frac{26mV}{I_E} = \frac{26mV}{3.05mA} = 8.5 \Omega$$

$$r_e = 8.5 \Omega$$

$$V_C = 12 - (2.2k + 60 \times 0.05mA) = 5.4V$$

$$V_E = 0$$

$$V_{CE} = V_C - V_E = 5.4 - 0 = 5.4 > 0.2$$

$$\text{and } I_C = 3mA \neq 0$$

active region. لطريقين

أخيرا نتأكد من فرضه

$$I_C \neq 0, V_{CE} > 0.2$$

$V_{BE} > 0.7 \rightarrow$ Forward Junction
and $V_{BC} < 0.7 \rightarrow$ Reverse Junction.

$$\therefore I_C \neq 0 \quad \text{and} \quad V_{CE} > 0.2 \text{ V}$$

\therefore The assumption, considered is correct and transistor is located in active region.

other
method \rightarrow

$$V_{BE} = 0.7 \text{ V (Forward)}$$

$$V_{BC} = V_B - V_C = 0.7 - 5.4 = -4.7 \text{ V} < 0.7 \text{ (reverse)}$$

} active
region

3

For determining $r_e \rightarrow$ make DC analysis

assume transistor is located in active region ($V_{BE} = 0.7$)

\therefore base current is so small, hence V_B can be obtained by applying voltage divider at base point as follows:-

$$V_B = \frac{16 \times 4.7k}{39k + 4.7k} = 1.7 \text{ Volt.}$$

$$V_{BE} = V_B - V_E$$

$$0.7 = 1.7 - V_E \rightarrow V_E = 1 \text{ Volt.} \rightarrow I_E = \frac{V_E}{R_E} = \frac{1}{1.2k}$$

$$I_E = 0.83 \text{ mA}$$


$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{0.83 \text{ mA}}$$

$$\boxed{r_e = 31 \Omega}$$

خطوة مهمة
عليها يرجع \rightarrow check assumption

$$\left. \begin{array}{l} 1 \text{ } I_C = \beta I_B \approx I_E = 0.83 \text{ mA} \neq 0 \\ V_{CE} = 16 - 0.83 \text{ mA} [3.9k + 1.2k] \\ = 11.8 \text{ Volt.} > 0.2 \text{ Volt} \end{array} \right\} \rightarrow \text{active region}$$
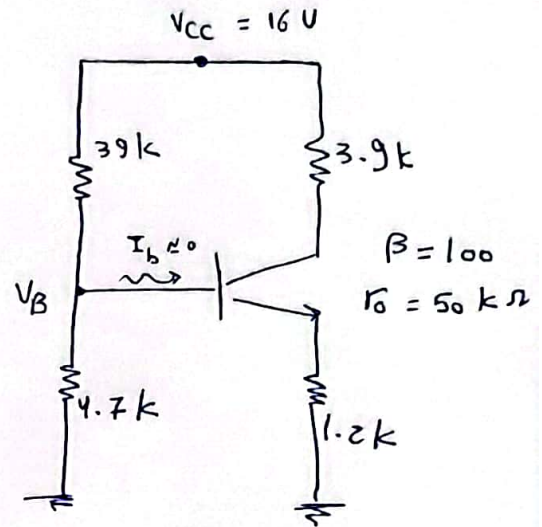
$$\left. \begin{array}{l} 2 \text{ } V_{CE} = V_C - V_E \\ 11.8 = V_C - 1 \\ V_C = 12.8 \text{ V} \end{array} \right\} \begin{array}{l} V_{BE} \approx 0.7 \text{ (Forward)} \\ V_{BC} = 1.7 - 12.8 = -11.1 < 0.7 \text{ (Reverse)} \end{array} \rightarrow \text{active region.}$$



4

r_e is computed from DC analysis to be used in AC analysis:
as follows: - assume $V_{BE} = 0.7$ (active region) then check

Apply KVL at left Loop: -

$$V_0 - 390k \times I_B - 0.7 - 1.2k(\beta + 1)I_B = 0$$

$$I_B = \frac{V_0 - 0.7}{390k + (1.2k \times 141)} = 0.0345 \text{ mA}$$


$$= 34.5 \mu\text{A}$$

$$I_E = (\beta + 1) \times I_B = (140 + 1) \times 0.0345$$

$$I_E = 4.9 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{4.9 \text{ mA}} = 5.3 \Omega$$

نستخدم في
الكسب الكلي $r_e = 5.3 \Omega$

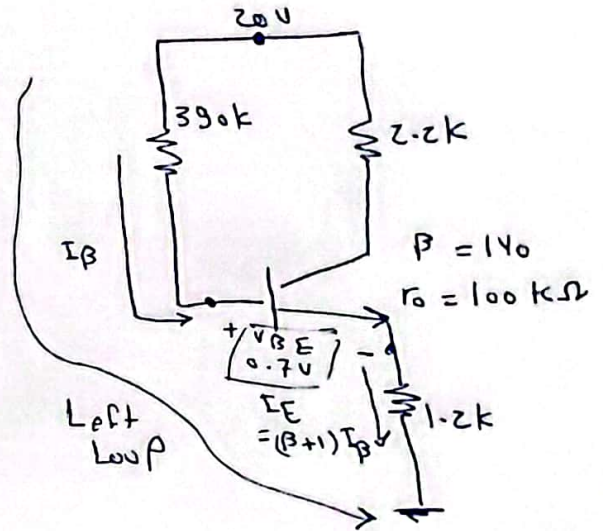

Finally \rightarrow check active region assumption.

$$V_{CE} = V_0 - 4.9 [2.2k + 1.2k] = 3.34 \text{ Volt} > 0.2$$

and $I_C \approx I_E = 4.9 \text{ mA} \neq 0$

\rightarrow active region

$$\begin{aligned} V_E &= I_E R_E \\ V_B &= V_{BE} + V_E \\ V_C &= V_{CE} + V_E \end{aligned}$$

(Forward) V_{BE}
(Reverse) V_{BC}

أو بطريقة

61

* DC analysis to compute r_e

* assume $V_{BE} = 0.7V$, considering transistor region is active

$$22 - 330k \times I_B - 0.7 - (1.2 + 0.47)k \times (\beta + 1)I_B \quad \text{Left Loop} = 0$$


$$I_B = \frac{22 - 0.7}{330k + (81 \times 1.67k)} = \frac{21.3}{135.27k}$$

$$I_B = 0.0458 \text{ mA} = 45.8 \mu A$$

$$I_E = (\beta + 1) \times I_B = (80 + 1) \times 0.0458$$

$$I_E = 3.7 \text{ mA}$$
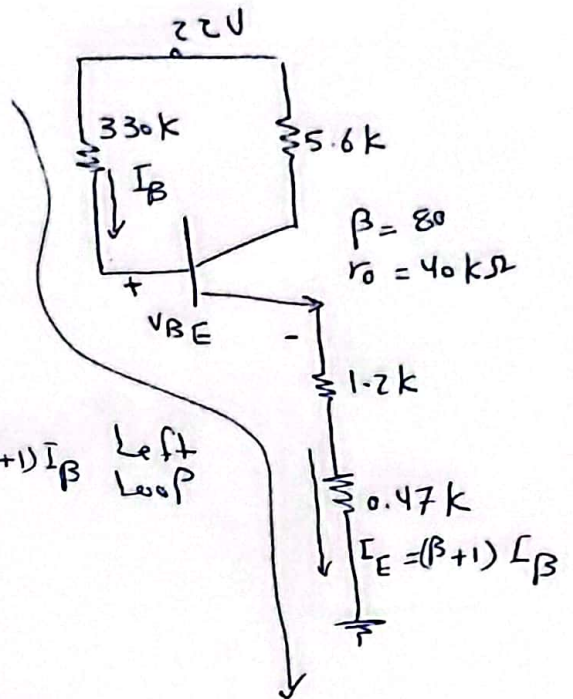
$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{3.7 \text{ mA}} \rightarrow \boxed{r_e = 7 \Omega}$$



Finally → check the assumption:-

$$I_C \approx I_E \approx 3.7 \text{ mA} \neq 0$$

ok at right loop:-

$$V_{CE} = 22 - 3.7 \text{ mA} [5.6k + 1.2k + 0.47k]$$

$$V_{CE} = -4.9 \text{ Volt}$$

7

assume transistor is in active region hence $V_{BE} = 0.7V$

apply KVL at loop ① :-

$$-390k \times I_B - 0.7 - 5.6k \times (\beta + 1) I_B = 0$$

$$-0.7 + 8 = [390 + (121 \times 5.6)] I_B$$

$$I_B = \frac{-0.7 + 8}{1068k} = 0.0068 \text{ mA}$$

$$I_B = 6.8 \mu A$$

$$I_E = (\beta + 1) \times I_B$$

$$= (120 + 1) \times 0.0068$$

$$I_E = 0.8 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{0.8 \text{ mA}} = 32.5 \Omega$$

$$r_e = 32.5 \Omega$$


→ check assumption (active region)

$$* I_C \approx I_E = 0.8 \text{ mA} \neq 0$$

$$* V_{CE} = 12 - 0.8 \text{ mA} \times 5.6k + 8$$

$$V_{CE} = 15.5 \text{ volt}, > 0.2 \text{ V}$$


active region

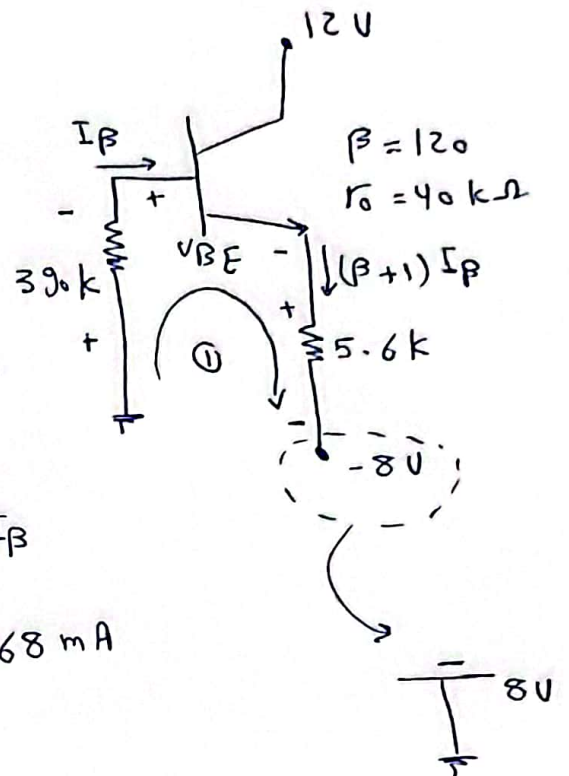

8

* DC analysis to compute r_e

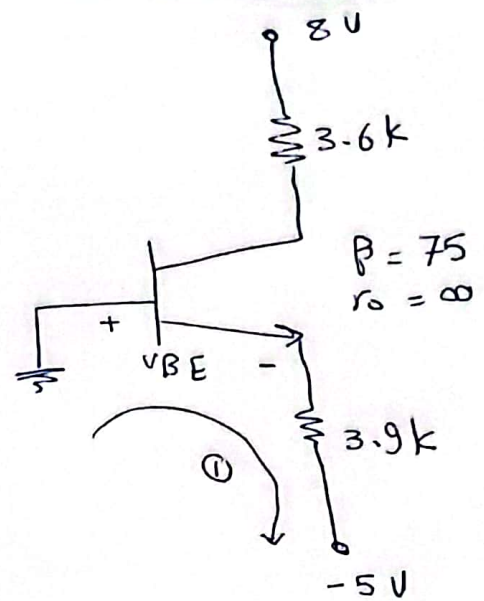* assume transistor is in active region $\xrightarrow{\text{hence}}$ $V_{BE} = 0.7V$
then check this assumption finally.



apply KVL at Loop ① :-

$$-0.7 - 3.9k \times I_E + 5 = 0$$

$$I_E = \frac{-0.7 + 5}{3.9k} = 1.1mA$$

$$\rightarrow r_e = \frac{26mV}{1.1mA}$$

$$\boxed{r_e = 23.6 \Omega}$$

\longrightarrow check whether the first assumption is true or false

$$I_C \approx I_E \approx 1.1mA \neq 0 \longrightarrow \underline{\underline{1}}$$

apply KVL at right loop :-

$$8 - 1.1mA \times [3.6k + 3.9k] + 5 = V_{CE}$$

$$V_{CE} = 4.75 > 0.2V \longrightarrow \underline{\underline{2}}$$

From 1 and 2
transistor is in active region and the previous assumption is correct.

9


DC analysis to compute r_e

→ assume active region ($V_{BE} = 0.7V$)

apply KVL at left loop:-

$$12 - 3.9k \times (\beta + 1) I_B - 220k \times I_B - 0.7 = 0$$

121

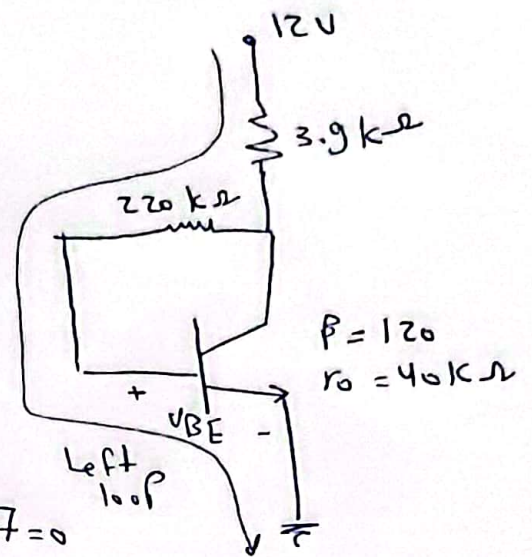

$$I_B = \frac{12 - 0.7}{[3.9k \times 121] + 220k} = 0.0163 \text{ mA}$$

$$= 16.3 \mu A$$

$$I_E = (\beta + 1) \times I_B = (120 + 1) \times 0.0163$$

$$I_E = 1.97 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.97 \text{ mA}}$$

$$r_e = 13.19 \Omega$$

→ check the first assumption, concerned the transistor region.

$$I_C \approx I_E \approx 1.97 \text{ mA} \neq 0 \rightarrow \textcircled{1}$$

apply KVL at right loop:-

$$V_{CE} = 12 - 3.9k \times 1.97 \text{ mA}$$

$$= 4.3 \text{ V} > 0.2 \text{ V} \rightarrow \textcircled{2}$$

assumption is correct and transistor is in active region.

or check by another method:- V_{BE} Forward
 V_{BC} Reverse