

Ac Voltmeter: The instrument, which is used to measure the Ac Voltage across any two points of electric circuit

classification of Ac Voltmeter ..

- ① Average Responding [using HWR & FWR]
- ② Peak Responding
- ③ RMS Responding


If the Ac voltmeter consists of rectifier, then it is said to be **rectifier based Ac Voltmeter**

Types of rectifier based Ac Voltmeter:

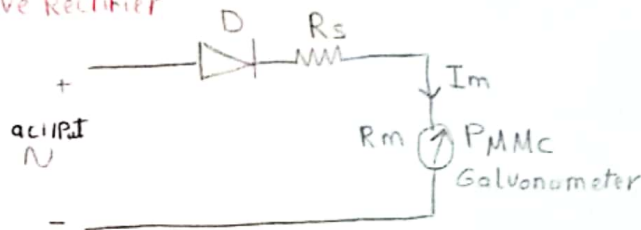- a) Ac voltmeter using Half Wave Rectifier.
- b) Ac voltmeter using Full Wave Rectifier.

① **Ac Voltmeter using Half Wave Rectifier**

D conducts only during positive half cycle



The rms value of sinusoidal (Ac) i/p Voltage signal is

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\therefore V_m = \sqrt{2} V_{rms} = 1.414 V_{rms}$$

$$V_m = V_P = \text{Peak Voltage}$$

$V_m \rightarrow$ is the maximum value of sinusoidal (Ac) i/p Voltage signal

The dc or average value of the Half wave rectifier o/p signal is

$$V_{av} = V_{dc} = \frac{V_m}{\pi}$$

$$V_m = 1.414 V_{rms}$$

$$\therefore V_{dc} = \frac{1.414 V_{rms}}{\pi} = 0.45 V_{rms}$$

\therefore The Ac voltmeter produces an o/p voltage, which is equal to 0.45 times the rms value of the sinusoidal (Ac) i/p Voltage signal.


The value of series multiplier (R_s) can be obtained

$$R_{se} = \frac{E_{dc}}{I_{dc}} - R_m$$

$$= \frac{0.45 E_{rms}}{I_{dc}} - R_m$$

$I_{dc} \rightarrow$ Full scale deflection current

② AC Voltmeter using Full wave Rectifier

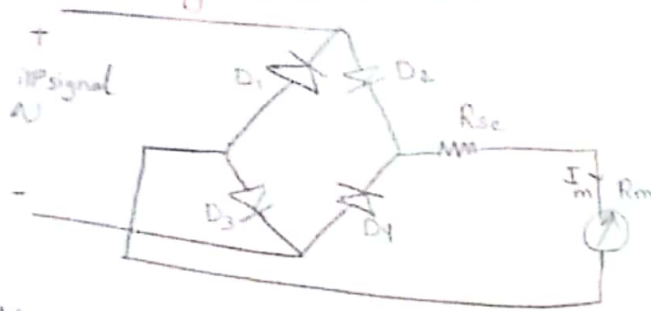

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$- V_m = V_p = 1.414 V_{rms}$$

$V_m \rightarrow$ maximum value of a/c signal

$$V_{av} = V_{dc} = \frac{2 V_m}{\pi} = \frac{2 \times 1.414 V_{rms}}{\pi} = 0.9 V_{rms}$$

$V_{av} \neq V_{dc} \rightarrow$ average or dc value of the full wave rectifier a/c signal.

The multiplier resistance can be obtained as

$$R_{se} = \frac{E_{dc}}{I_{dc}} - R_m = \frac{0.9 E_{rms}}{I_{dc}} - R_m$$

Average Responding AC voltmeter

\rightarrow The scale on AC voltmeters are ordinarily calibrated in rms values of sinusoidal wave form.

$$\text{Form Factor } (k_f) = \frac{V_{rms}}{V_{avg}}$$

For Avg Responding AC voltmeter using FWR

$$k_f = \frac{V_{rms}}{V_{avg}} = \frac{V_{rms}}{0.9 V_{rms}} = 1.11$$

1. a.c. voltmeter using **HWR** $\& I_{dc} = 1 \text{ mA}$ $\& R_m = 200 \Omega$ $\& E_{rms} = 10 \text{ V}_{rms}$
 Calculate the multiplier resistance (R_s).

Solution

$$R_s = \frac{E_{dc}}{I_{dc}} - R_m = \frac{0.45 E_{rms}}{I_{dc}} - R_m$$

$$= \frac{0.45 \times 10}{1 \times 10^{-3}} - 200 \Omega = 4300 \Omega = 4.3 \text{ k} \Omega \#$$

2. a.c. voltmeter uses **FWR** $\& I_{dc} = 2 \text{ mA}$ $\& R_m = 500 \Omega$ $\& E_{rms} = 10 \text{ V}_{rms}$
 Calculate multiplier resistance R_s .

Solution

a.c. voltmeter uses FWR

$$\therefore E_{dc} = 0.9 E_{rms}$$

$$R_s = \frac{0.9 E_{rms}}{I_{dc}} - R_m = \frac{0.9 \times 10}{2 \times 10^{-3}} - 500 \Omega = 4000 \Omega = 4 \text{ k} \Omega \#$$

3. Average responding voltmeter


calculate k_f of square wave $\&$ error in the meter reading

Solution

$$E_{rms} \text{ of square wave} = \sqrt{\frac{1}{T} \int_0^T E^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T E_m^2 dt} = \sqrt{\frac{1}{T} E_m^2 T}$$

$$= E_m$$

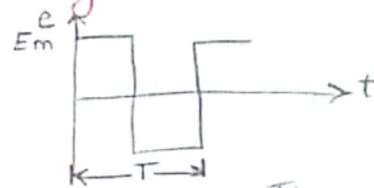

$$V_{avg} = \frac{2}{T} \int_0^{T/2} V_m dt$$

$$E_{avg} = \frac{2}{T} E_m \frac{T}{2} = E_m$$

Average Value E_{avg} For square wave = E_m

$$\therefore k_f = \frac{\text{rms Value}}{\text{average Value}} = \frac{E_{rms}}{E_{avg}} = \frac{E_m}{E_m} = 1$$

\therefore scale is calibrated in terms of the rms value of purely sinusoidal waveform

$$k_f \text{ For sinusoidal} = \frac{E_{rms}}{E_{avg}} = \frac{E_{rms}}{0.9 E_{rms}} = 1.11$$


$$\therefore E_{rms} = 1.11 E_{avg} \text{ For sinusoidal}$$

$$E_{rms} = E_{avg} \text{ For square wave}$$

\therefore reading on voltmeter will be higher by factor $\frac{k_f \text{ For sinusoidal}}{k_f \text{ For square wave}} = \frac{1.11}{1} = 1.11$

$$\therefore \text{Percentage error in the reading} \quad \% = \frac{\text{true} - \text{measured}}{\text{True}} \times 100 = \frac{1 - 1.11}{1} \times 100 = -11\% \#$$

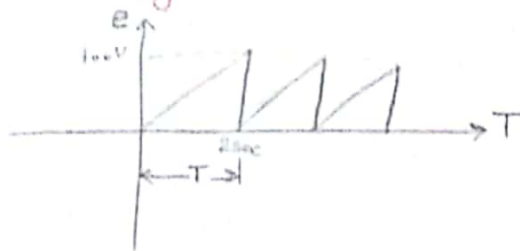4) calculate the Percentage error in the reading



$$e = At$$

$A \rightarrow$ slope of ramp

$$A = \frac{100 - 0}{2 - 0} = 50$$

$$e = 50t \quad 0 \leq t \leq T$$

$$E_{rms} = \sqrt{\frac{1}{T} \int_0^T e^2 dt} = \sqrt{\frac{1}{T} \int_0^T (50t)^2 dt}$$

$$= \sqrt{\frac{1}{T} (50)^2 \frac{T^3}{3}} = \sqrt{\frac{T^2}{3} (50)^2} = \frac{50T}{\sqrt{3}}$$

$$T = 2 \text{ sec}$$

$$\therefore E_{rms} = \frac{100}{\sqrt{3}} \text{ V}$$

$$E_{av} = \frac{1}{T} \int_0^T e dt = \frac{1}{T} \int_0^T 50t dt = \frac{1}{T} \frac{50T^2}{2} = 25T = 25 \times 2 = 50 \text{ V}$$

$$k_f (\text{form factor}) = \frac{E_{rms}}{E_{avg}} = \frac{100/\sqrt{3}}{50} = 1.155 \quad \text{For sawtooth}$$

$$k_f \text{ for sinusoidal wave} = 1.11$$

$$\therefore \text{The meter will read less by factor } \frac{k_{f \text{ sine}}}{k_{f \text{ sawtooth}}} = \frac{1.11}{1.155} = 0.961$$

$$\therefore \text{Percentage error} = \frac{\text{True} - \text{measured}}{\text{True}} \times 100 = \frac{1 - 0.961}{1} \times 100 = 3.87\% \#$$

5) $I = 25 \text{ mA}$ $\&$ $R_m = 100 \Omega$ $\&$ 200 V_{rms} $\&$ Forward resistance of diode = 500Ω
 calculate the value of the series resistance to limit the current to the rated value.
 at the rated voltage

solution

\therefore a.c. voltmeter uses the bridge \therefore FWR

$$E_{dc} = 0.9 E_{rms}$$

$$\therefore R_s = \frac{E_{dc}}{I_{dc}} - R_m =$$

\therefore diode forward resistance = 500Ω $\&$ due to the bridge configuration, two diodes will be in series at a time $\therefore R_D = \text{diode resistance} = 2 R_f = 1000 \Omega$

$$\therefore R_m = R_m + R_D = 100 + 1000 = 1100 \Omega$$

$$\therefore R_s = \frac{0.9 \times 200}{2 \times 10^{-3}} - 1100 = 6100 \Omega \#$$