



Electronics and Electrical Communications Engineering Dep.




2nd Year / 2nd Term

Electronic Measurements (2)

Lecture (2)

By Dr. Hager Fouda

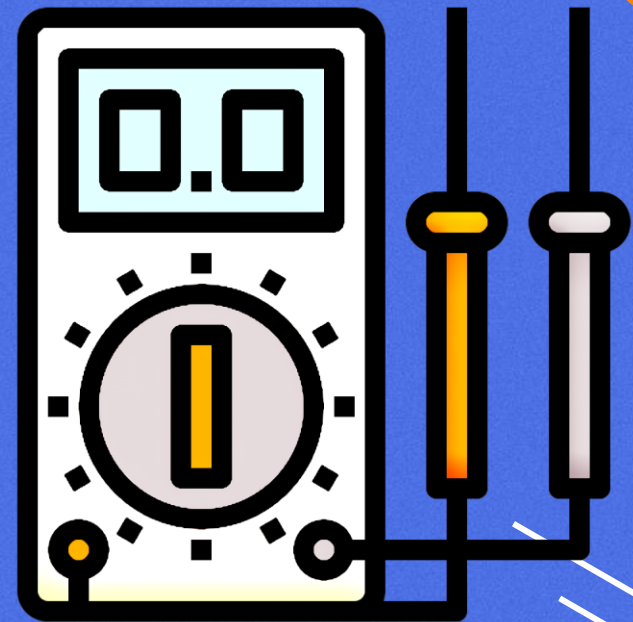


Lecture Content

- ☐ AC Voltmeter
- ☐ AC Voltmeter Reading
- ☐ AC Voltmeter using Rectifier
- ☐ Rectifier basic Type AC Voltmeter
- ☐ Average Responding Voltmeter
- ☐ Peak Responding Voltmeter
- ☐ True Rms Responding Voltmeter
- ☐ Quasi Rms Detection
- ☐ AC Differential Voltmeter

Ac Voltmeter

❑ Electronic Analog Ac Voltmeter

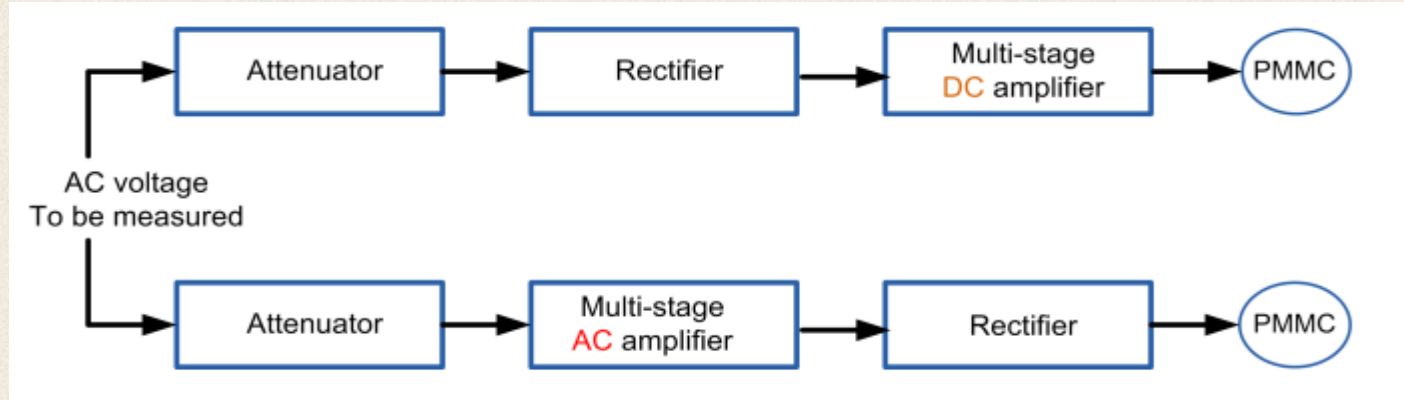

- ❑ The main difference between AC voltmeter circuit and DC voltmeter circuit is **the usage of a rectifier**.
- ❑ The rectifier is used in order to transform the AC voltage into DC voltage.

Ac Voltmeter

AC Electronic Analog Voltmeter

- ☐ AC Voltmeter Using Rectifier
 - Rectification before Amplification
 - Amplification before Rectification
 - Using Half Wave Rectifier (HWR)
 - Using Full Wave Rectifier (FWR)
- ☐ Average Responding Voltmeter
- ☐ Peak Responding Voltmeter
- ☐ True RMS Voltmeter
- ☐ Quasi RMS Detection
- ☐ AC Differential Voltmeter

Ac Voltmeter Reading

1. Peak value (V_m)

It is the maximum value attained by the AC waveform either in the positive half cycle or negative half cycle. It is also known as **amplitude**.

2. Average value

- ❑ It is the average of all the instantaneous value over a period of **a half one complete cycle**.
- ❑ For **symmetrical** AC quantity, the average value over a complete cycle is zero. Hence average value is calculated over a half cycle.
- ❑ If the AC quantity is continuous then average value can be expressed mathematically using an integration.

$$V_{ave} = \frac{2}{T} \int_0^{T/2} v_{in} dt$$

Ac Voltmeter Reading

3. Root mean squared (RMS) value

- ❑ RMS” stands for Root Mean Square, and is a way of expressing an AC quantity of voltage or current in terms functionally equivalent to DC.
- ❑ For example, 10 volts AC RMS is the amount of voltage that would produce **the same** amount of heat dissipation across a resistor of given value as a 10 volt DC power supply.
- ❑ The RMS value is the effective value of a varying voltage or current.
- ❑ It is the equivalent steady DC (constant) value which gives the same effect.
- ❑ For example, a lamp connected to a 6V RMS AC supply will shine with the same brightness when connected to a steady 6V DC supply.



$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v_{in}^2 dt}$$

Ac Voltmeter Reading

- ❑ For purely **sinusoidal** quantity

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

RMS Voltage Equivalent

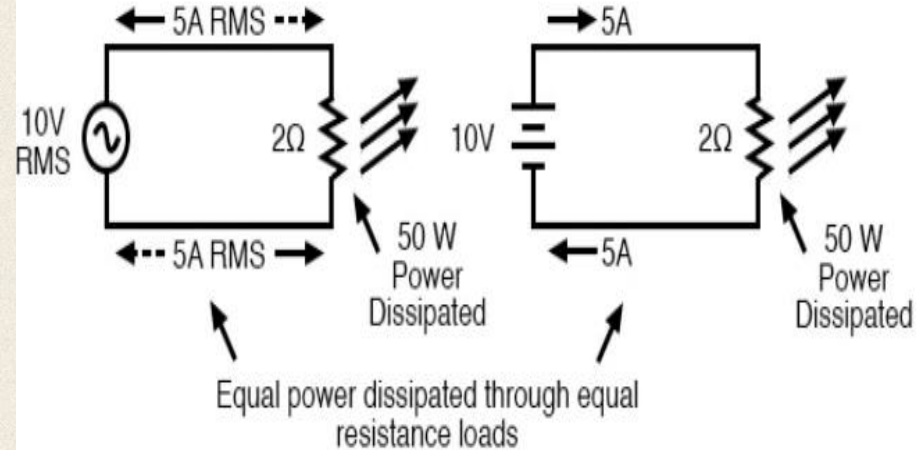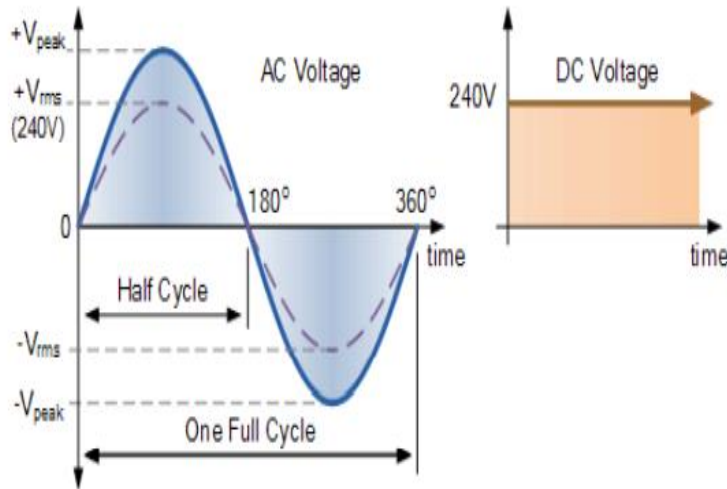

An RMS voltage produces the same heating effect as the same DC voltage

Ac Voltmeter Reading


- ❑ The scale on AC voltmeters are ordinarily **calibrated** in rms values of a sinusoidal wave form.

$$\text{Form Factor} = \frac{\text{rms value}}{\text{average value}}$$

$$\text{Peak Factor} = \text{crest factor} = \frac{\text{peak value}}{\text{rms value}}$$

- ❑ For purely sinusoidal quantity
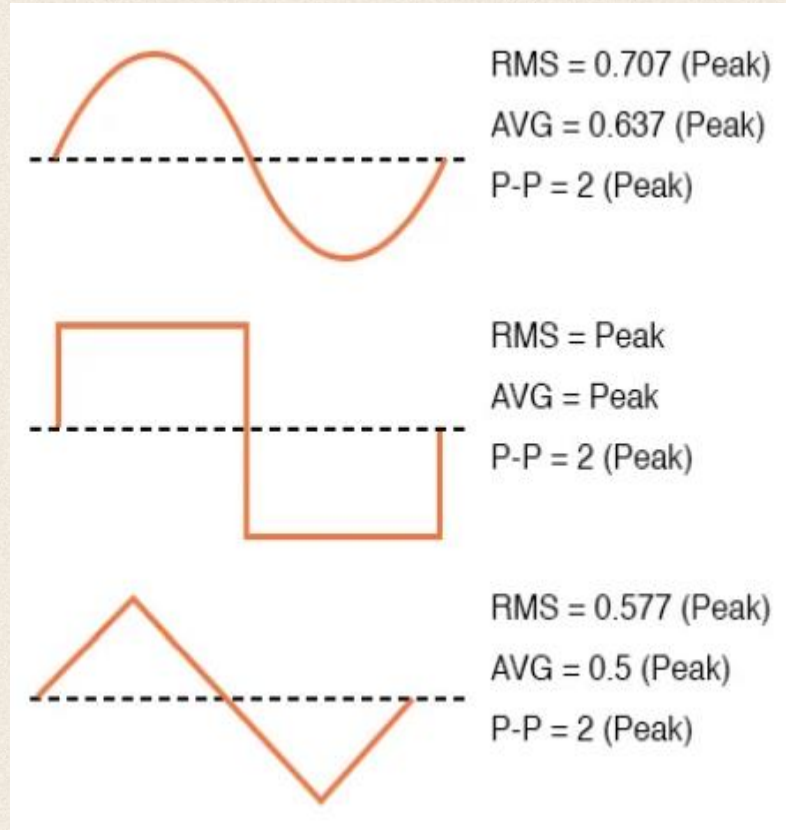
$$\text{Peak Factor} = \sqrt{2} = 1.414$$



Sensitivity of Voltmeters

$$\text{Sensitivity } (S) = \frac{1}{I_{FSD}} \Omega/V$$


- where I_{FSD} is the full scale deflection current
- ☐ It is also called **the ohm per volt rating** of the voltmeter.
- ☐ Internal resistance of the voltmeter can be obtained by:

$$R_m = \text{Maximum Voltage range} \times \text{sensitivity in } \Omega/V$$

- ☐ The sensitivity is useful in calculating **the multiplier resistance** values, **required for multi-range voltmeter**.


AC Voltmeter Using Rectifier

AC Voltmeter with First Amplification

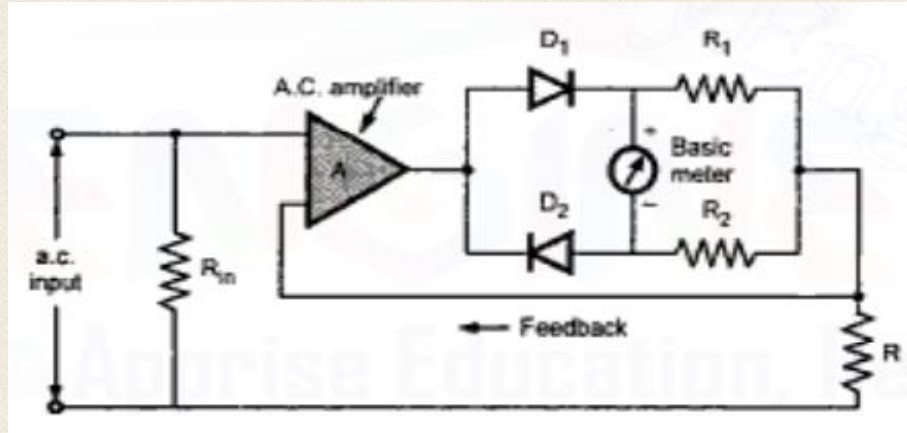

- ❑ The AC amplifier requires a high open loop gain and large amount of negative feed back to **overcome the non-linearity** of the rectifier diodes

AC Voltmeter with First Rectification

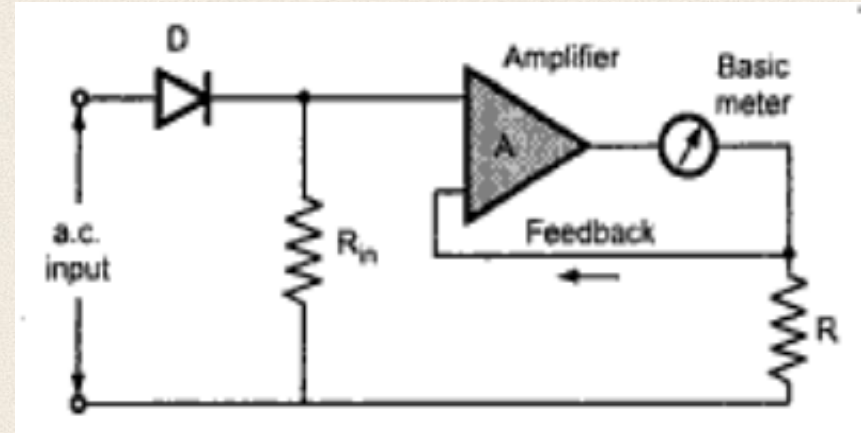


- ❑ This approach ideally requires a DC amplifier **with zero drift** characteristics and a DC meter movement with high sensitivity.

AC Voltmeter Using Rectifier

Diode using limitation

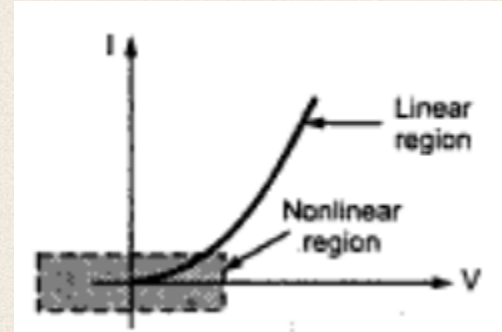1. The diode are **nonlinear** device particularly at low values of the forward current. Due to this nonlinearity, the meter scale is also nonlinear and is crowded at the **lower end of a low range voltmeter**. In this region, the meter sensitivity is also very low because of **high** forward resistance of the diode.
2. Depending of diode characteristics on **temperature** is also an important factor in AC voltmeters.
3. The rectifier shows the **capacitance properties** under reverse biased and tends to bypass **high** frequencies. The meter reading may have error due to such effect of the order of 0.5% decrease for every 1KHz rise in the frequency.




Basic Rectifier Type AC Voltmeter

AC Voltmeter Using HWR

- ❑ The diode conducts only for half cycle and meter movement is **bypassed** for another cycle.
- ❑ The rectified DC is a pulsating DC, hence the meter will deflect proportional to the **average value**.
- ❑ The pointer will deflect for a full scale if 10 V dc is applied and 4.5 V when a 10 V_{rms} sinusoidal signal is applied.
- ❑ This means that an ac voltmeter is less sensitive than a dc voltmeter. As $V_{ave} = V_{dc} = \frac{V_m}{\pi} = 0.45 V_{rms}$
- ❑ For half wave, the value of **the multiplier resistor** is obtained as:

$$R_s = \frac{E_{dc}}{I_{dc}} - R_m = \frac{0.45 E_{rms}}{I_{dc}} - R_m$$

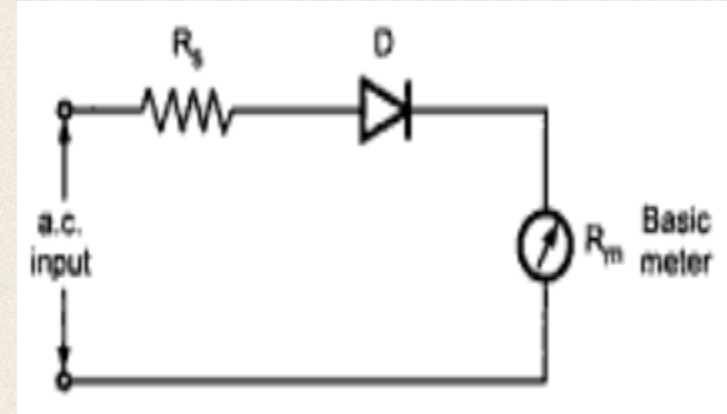- where $I_{dc} = I_{FSD}$ is the full scale deflection current.




Basic Rectifier Type AC Voltmeter

AC Voltmeter Using FWR

- As $V_{ave} = V_{dc} = \frac{2V_m}{\pi} = 0.9 V_{rms}$: we can see that a $10 V_{rms}$ voltage is equal to a $9 V_{dc}$ for full scale deflection, i.e. the pointer will deflect to 90% of full scale.

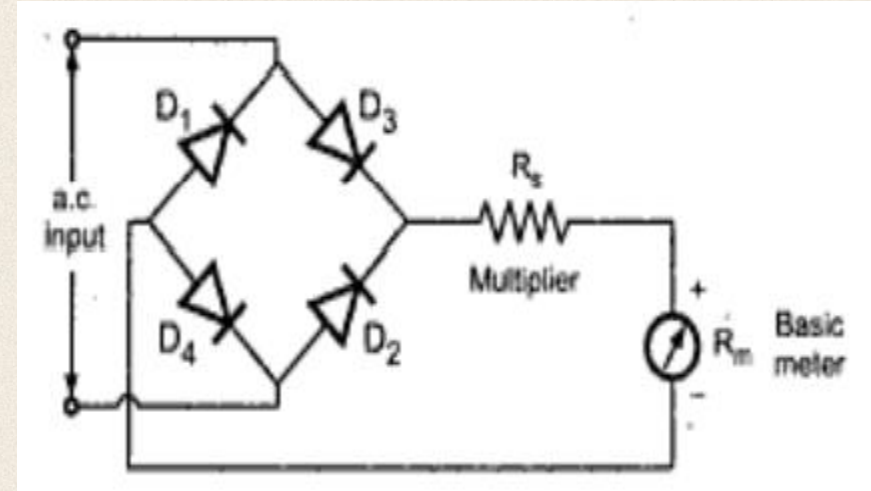
Sensitivity of AC voltmeter
= 0.9 × Sensitivity of DC voltmeter



- **For full wave**, the value of the multiplier resistor is obtained as:

$$R_s = \frac{E_{dc}}{I_{dc}} - R_m = \frac{0.9 E_{rms}}{I_{dc}} - R_m$$

Average Responding Voltmeter

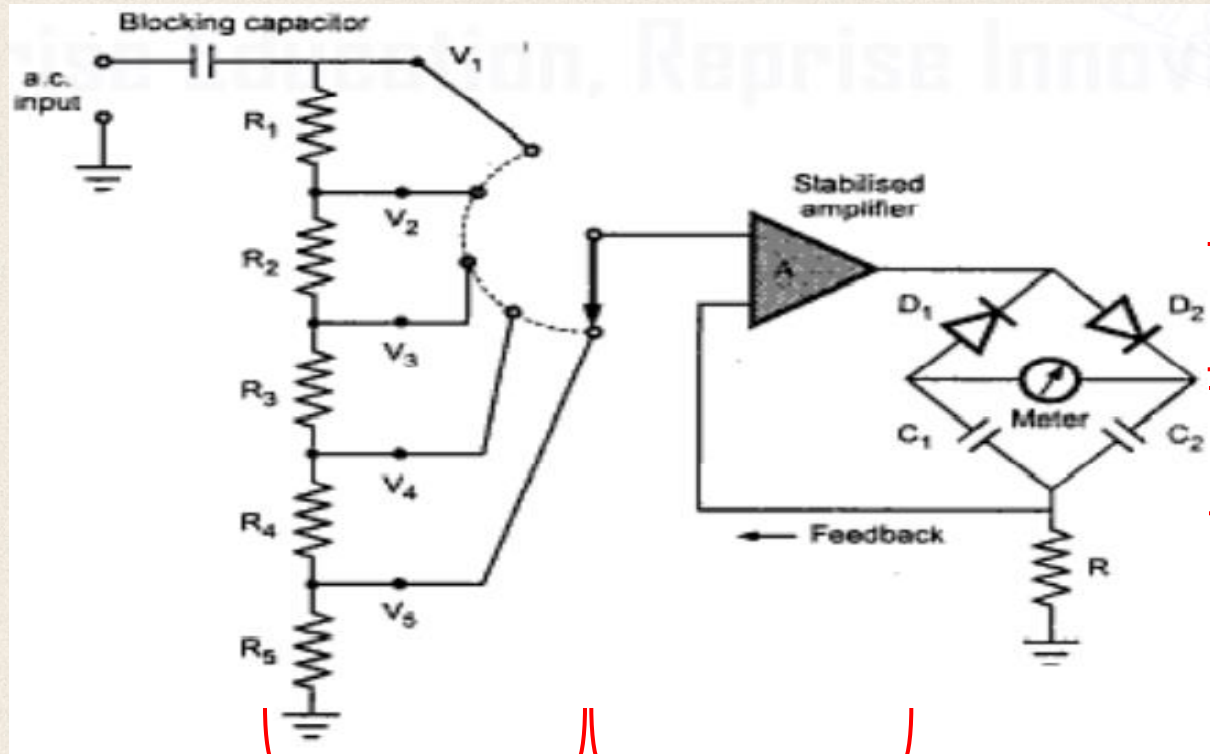

Rectification

Integration

Range selection

Amplification

Average Responding Voltmeter

- ❑ Blocking capacitor used at the input side **blocks** any dc component in the input voltage.
- ❑ The ac input applied is **first amplified** with the help of high gain stabilized amplifier.
- ❑ This voltage is then **rectified** using diodes D1 and D2.
- ❑ The rectified voltage is fed to a **dc milliammeter** used as a measuring meter.
- ❑ The current obtained from the rectifier is **averaged** by using **a filter** to produce a steady state deflection of the meter pointer.
- ❑ The dc milliammeter is **calibrated in term of rms value** of the input voltage.
- ❑ The meter responds to **the average reading** of the input, hence called the average responding meter.
- ❑ The capacitor C1 and C2 in the rectifier circuit act as **filter** capacitors. These capacitors also act as the **coupling capacitors** in the feedback path.

Average Responding Voltmeter

❑ Large amount of **negative feedback** is used for the amplifier to:


- Ensure stability for measurement accuracy.
- Increase the frequency range of the instrument.
- Minimize the effect of diode nonlinearity.
- Compensate any changes in the meter impedance.

Advantages

Disadvantages


- Waveforms which are distorted, nonuniform, nonsinusoidal including hum or noise, **produce errors** in the reading.
- Accuracy of the meter depends not only on the amplitude but also on the phase of the harmonic contents at the input side.

Peak Responding Voltmeter

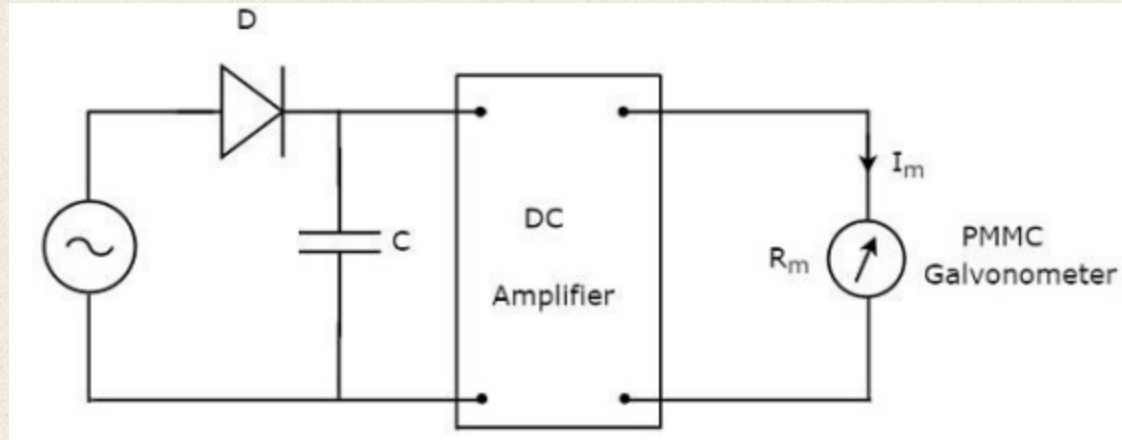

- ❑ The primary difference between the peak-responding voltmeter and the average responding voltmeter is **the usage of a storage capacitor** with the rectifying diode.
- ❑ The diode present in the above circuit is used for rectification purpose. So, the diode converts AC voltage signal into a DC voltage signal.
- ❑ The capacitor charges to the peak value of this DC voltage signal.

Peak Responding Voltmeter

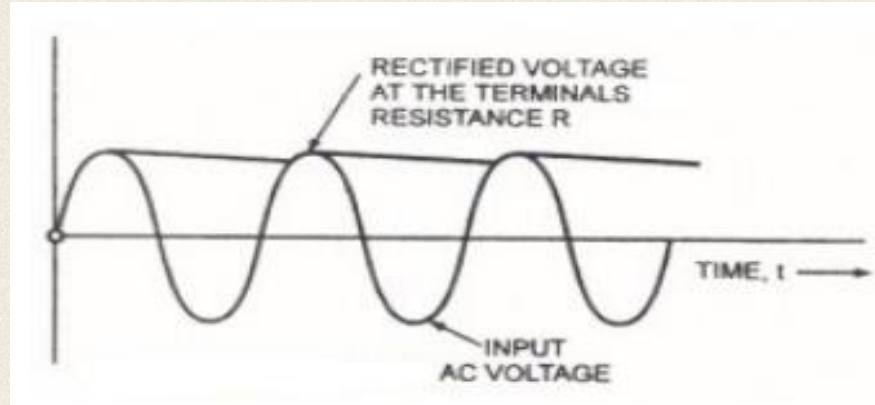

- ❑ During positive half cycle of AC voltage signal, the diode conducts and the capacitor **charges to the peak value** of AC voltage signal.
- ❑ When the value of AC voltage signal is less than this value, the diode will be reverse biased.
- ❑ Thus, the capacitor will discharge through the resistor R of DC amplifier till the next positive half cycle of AC voltage signal.
- ❑ When the value of AC voltage signal is greater than the capacitor voltage, the diode conducts and the process will be repeated.

Peak Responding Voltmeter

- ❑ We should select the component values in such a way that the capacitor **charges fast and discharges slowly**.
- ❑ As a result, the meter always responds to this capacitor voltage, i.e. the peak value of AC voltage.
- ❑ The condition is: $RC \gg T$



Disadvantages

- Harmonic distortion in the input causes errors.
- The instrument has limited sensitivity due to imperfect and nonlinear diode characteristics.
- Error is introduced if the input waveform is not symmetrical.

True RMS Responding Voltmeter

Thermocouple

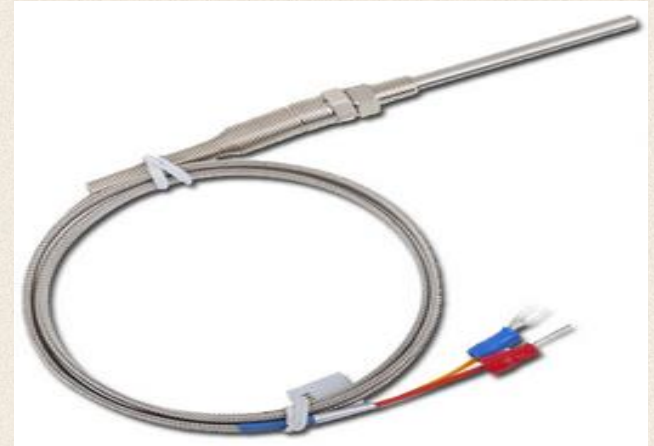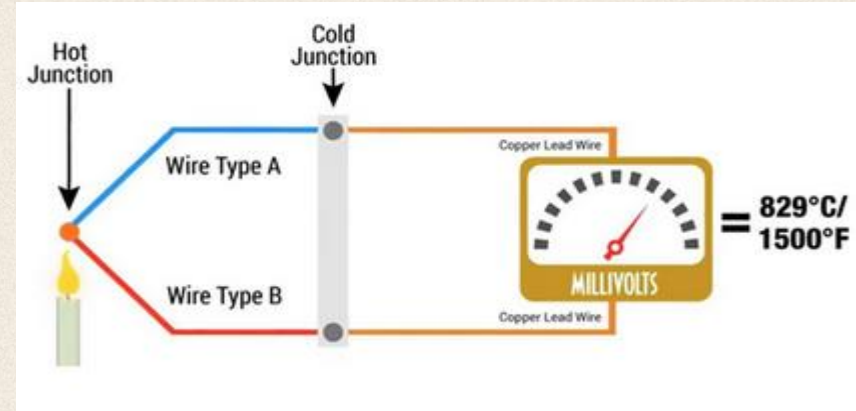- ❑ A Thermocouple is a sensor used **to measure temperature.**
- ❑ It consists of two wire legs made from different metals.
- ❑ The wire legs are welded together at one end, creating a junction.
- ❑ This junction is put where the temperature is measured.
- ❑ When the junction experiences a change in temperature, **a voltage is created.**



True RMS Responding Voltmeter


- ❑ The heating power $\propto V_{rms}^2$
- ❑ $Power = \frac{V_{rms}^2}{R_{heater}}$, where R_{heater} is the heater resistance.
- ❑ Thermocouple output voltage $V_{out} \propto \text{heat} \propto \text{power}$.
- ❑ $V_{out} = \frac{k_t V_{rms}^2}{R_{heater}}$
- ❑ k_t is the proportionality constant depends on the distance between the heater and the thermocouple hot-junction and also on the materials used in the heater and thermocouple.

True RMS Responding Voltmeter

Working Principle of True RMS Responding AC Voltmeter

- ❑ **Complex** waveforms are most accurately measured with a **true RMS** responding voltmeter.
- ❑ This instrument produces a meter indication (deflection) by: sensing the waveform heating power (usually using a thermocouple) .
- ❑ The heating power is proportional to the square of the RMS value of the input waveform (voltage).
- ❑ This heating power can be measured by feeding an amplified version of the input waveform to the heater element of a thermocouple whose
- ❑ output voltage is then proportional to V_{rms}^2

True RMS Responding Voltmeter

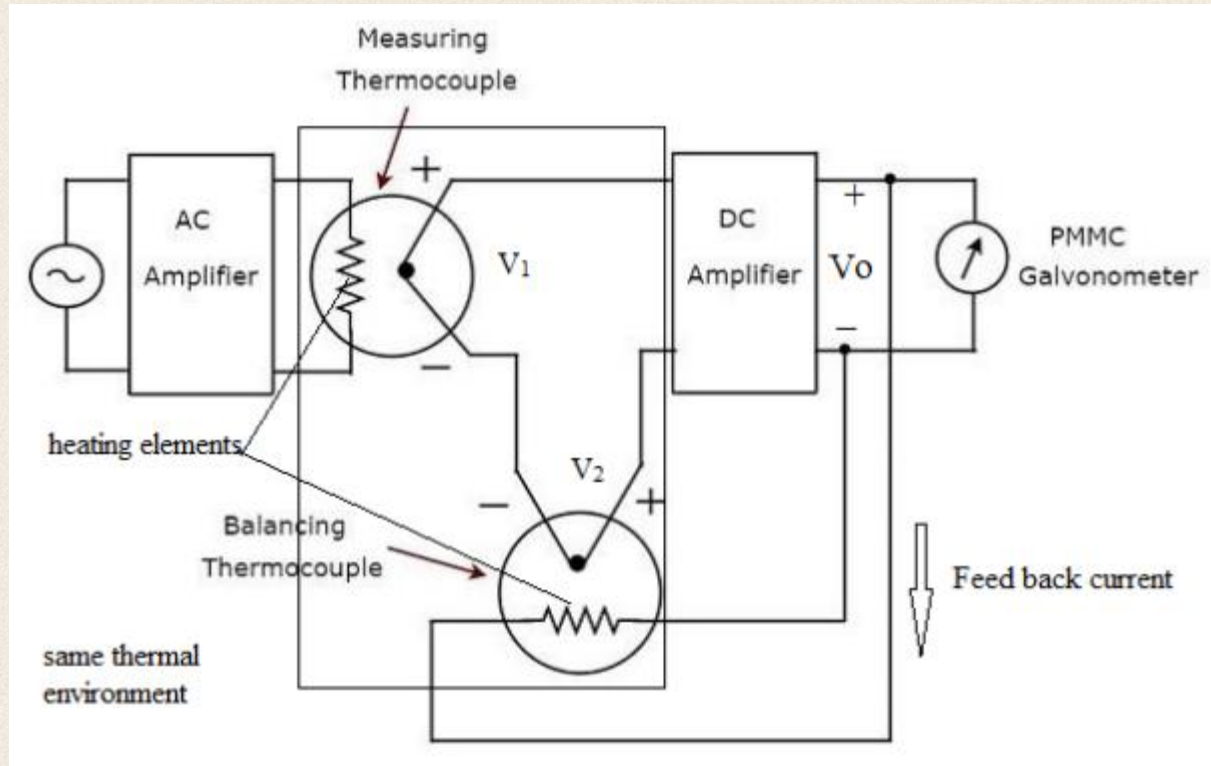

True RMS Responding Voltmeter

Factors that affect the reading accuracy

❑ Thermal radiation

Overcome by enclosing the heater and thermocouple **in the same** thermal environment, e.g., glass bubble.

❑ Non-linear characteristics of the thermocouple

- Overcome using balancing thermocouple where the effect of non-linear behavior of the thermocouple in the input circuit (measuring thermocouple) is **cancelled** by similar non-linear effects of the thermocouple in the feedback circuit (balancing thermocouple).
- Furthermore, the two thermocouples are placed in the same thermal environment. The two thermocouples balancing and measuring form a balanced bridge in the input circuit of the DC amplifier

True RMS Responding Voltmeter

- ❑ The unknown ac voltage is amplified and applied to the heating element of the measuring thermocouple.
- ❑ The application of heat produces an output voltage (V_1) that upsets the balance of the bridge.
- ❑ The dc amplifier amplifies the unbalanced voltage.
- ❑ The amplified voltage is fed back to the heating element of the balancing thermocouple, which heats the thermocouple to produce (V_2), such that the bridge is balanced again, i.e. the outputs of both the thermocouples are the same.
- ❑ At this instant, the DC current in the heating element of the feedback thermocouple is equal to the AC current in the input thermocouple.
- ❑ This DC current is therefore **directly proportional** to the effective, or RMS, value of the input voltage and is indicated on the meter movement in the output circuit of the DC amplifier.

True RMS Responding Voltmeter

□ In balanced condition of the bridge: $V_1 = V_2$.

where V_1 : is the output of the measuring thermocouple. and V_2 : is the output of the balancing thermocouple.

$$\square V_1 = k_1 V_{rms}^2$$

where V_{rms} is the RMS value of the input waveform.

$$\square V_2 = k_2 V_o^2$$

where V_o is the output DC voltage.

$$\square k_1 = k_2 = \frac{k_t}{R_{heater}}$$

□ Due to thermal environment used for the two thermocouples:

$$V_{rms}^2 = V_o^2 \rightarrow V_{rms} = V_o$$

□ The true RMS value is measured **independent** of the waveform of the ac input provided that, the peak amplitude of the ac input is within the dynamic range of the ac amplifier.

True RMS Responding Voltmeter

Advantages

- ❑ Nonlinear behavior is avoided by using two thermocouples placed **in the same** thermal environment.
- ❑ True rms value measured is **independent of the waveform of the ac input**, if the peak amplitude of the ac input is within the dynamic range of the ac amplifier.
- ❑ Voltages through a range of $100\ \mu V$ to $300\ V$ within a frequency range 10Hz to 10MHz can be measured.

Disadvantages


- ❑ Response of thermocouples is **very slow**, hence the overall response of the meter sluggish.
- ❑ Meter cost is **high** compared to average and peak responding meters.

Quasi rms Detection


- ❑ Rms value of waveform can be expressed as

$$V_{rms} = K_1 V_m + K_2 V_{ave}$$

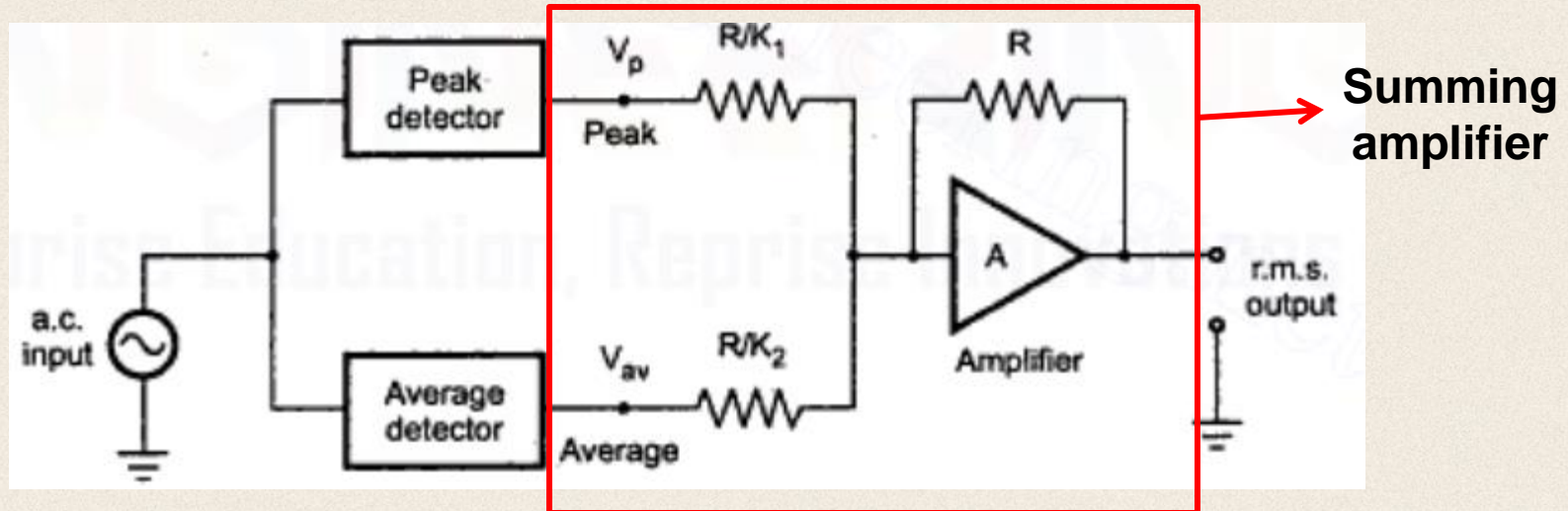- ❑ In this technique, rms value of the input waveform is measured by using **average and peak detectors**.



AC Differential Voltmeter

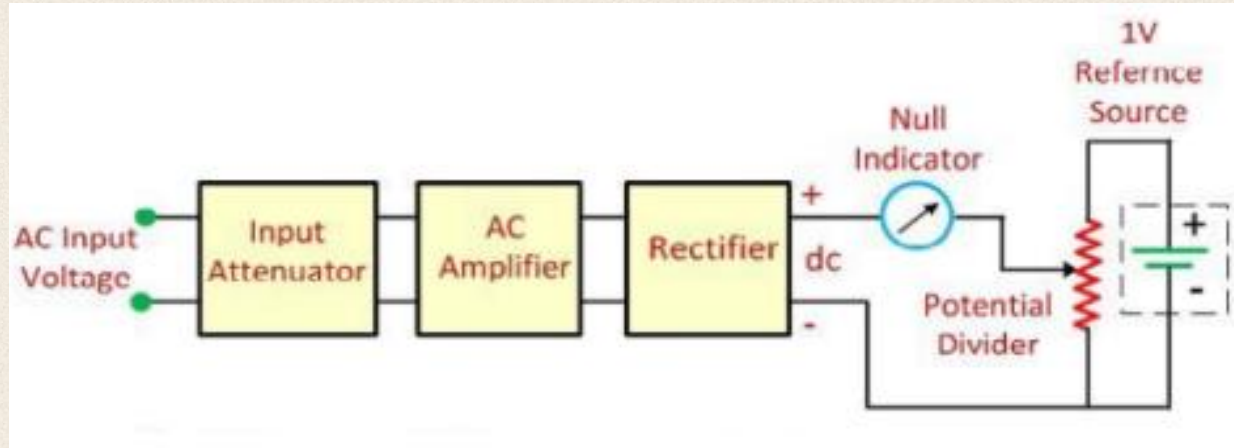

- ❑ The rectifying AC voltage compares with the standard DC voltage.
- ❑ The meter shows the null deflection when their magnitudes become equals.

Lecture References

1. Purkait, Prithwiraj. Electrical and electronics measurements and instrumentation. McGraw-Hill Education, 2013.
2. Kishore, K. Lal. Electronic Measurements and Instrumentation. Pearson Education India, 2009.
3. Dr. Nansy El-Shaer. Electronics and Electrical Communications Engineering Faculty of Engineering Tanta University. Electronic Analog Voltmeter lectures.

Thank you!

Any question?

You are welcome in Microsoft team chat